 




**METU EE 446
Computer Architecture
Laboratory**

Multi Cycle Processor Design



Laboratory Work 3 - Multi Cycle Processor Design

Objectives

This laboratory work aims to practice the design of a 32-bit multi-cycle processor. You will construct a datapath and a control unit of the multi-cycle processor like the one discussed in class. The designed processor will be able to execute all instructions in the given restricted instruction set.

During this laboratory work, you will further improve your hard-wired controller design skills by designing the controller unit of the multi-cycle processor. Finally, you will embed your design into the FPGA of the Nexys A7 board and experiment with it.

1 Preliminary Work

To fulfill the requirements of this laboratory work, the following tasks should be performed.

1.1 Reading Assignment

The laboratory manual, where the regulations and other useful information exist, is available on the ODTUClass course page. Read that manual thoroughly. If you feel unfamiliar with Verilog HDL programming and multi-cycle processor design, please refer to the corresponding lecture notes of the EE445 and EE446 courses, which are available on the course page.

1.2 Multi Cycle Processor Design with Verilog HDL (100% Credits)

For this laboratory work, you will design and implement a 32-bit multi-cycle processor that executes the instruction in multiple clock cycles. First, you will design its datapath and then implement the corresponding controller.

Before starting this lab, you should be familiar with the multi-cycle implementation of the processor described in lecture slides. The multi-cycle from the lecture notes is given in Figure 2. You will implement a multi-cycle processor very similar to the one in the lecture notes with a few extra instructions you should be familiar with from the previous laboratory.

The goal of a multi-cycle CPU is to reuse hardware modules across different cycles. Therefore, some components, such as the ALU, should appear only once in the datapath.

The processor you design will not support all ARM instructions but only a restricted set listed in Table 1. For all instructions, conditional logic of **EQ**, **NE**, and **AL** are required. Thus, you only need the "Zero" flag. Condition codes defined in ARM standards are shown in Figure 3. You will implement a shifting functionality for the second operand for data processing. Note that, in data-processing instructions, Rd can be R15.

Mnemonic	Name		Operation
ADD	Addition	add Rd,Rn,Rm	$Rd \leftarrow Rn + (Rm \text{ } sh \text{ } sham5)$
SUB	Subtraction	sub Rd,Rn,Rm	$Rd \leftarrow Rn - (Rm \text{ } sh \text{ } sham5)$
AND	Bitwise And	and Rd,Rn,Rm	$Rd \leftarrow Rn \& (Rm \text{ } sh \text{ } sham5)$
ORR	Bitwise Or	orr Rd,Rn,Rm	$Rd \leftarrow Rn (Rm \text{ } sh \text{ } sham5)$
MOV	Move to Register	mov Rd,Rm	$Rd \leftarrow (Rm \text{ } sh \text{ } sham5)$
MOV	Move to Register	mov Rd,rot-imm8	$Rd \leftarrow (imm8 \text{ } rr \text{ } rot < < 1)$
CMP	Compare	cmp Rd,Rn,Rm	$Z \leftarrow (Rn == Rm)$
STR	Store	str Rd,[Rn,imm12]	$Mem[Rn + imm12] \leftarrow Rd$
LDR	Load	ldr Rd,[Rn,imm12]	$Rd \leftarrow Mem[Rn + imm12]$
B	Branch	b imm24	$PC \leftarrow (PC + 8) + (imm24 < < 2)$
BL	Branch with Link	bl imm24	$PC \leftarrow (PC + 8) + (imm24 < < 2), R14 \leftarrow PC + 4$
BX	Branch and Exchange	bx Rm	$PC \leftarrow Rm$

Table 1: ISA to be implemented

Note: You will use the 32-bit ARM ISA format as shown in Figure 1. You can check any web resource for instructions not explained here, as we use standard ARM format.

You will need the following components to construct the datapath, all of which are given on ODTUClass
You must use the provided modules for the testbench to work

- One Instruction and Data memory (IDM)
- One Register file
- One ALU
- Registers
- Seven Segment Display Converter

- One Immediate Extender
- One Combinational Shifter
- Multiplexers
- Debouncer

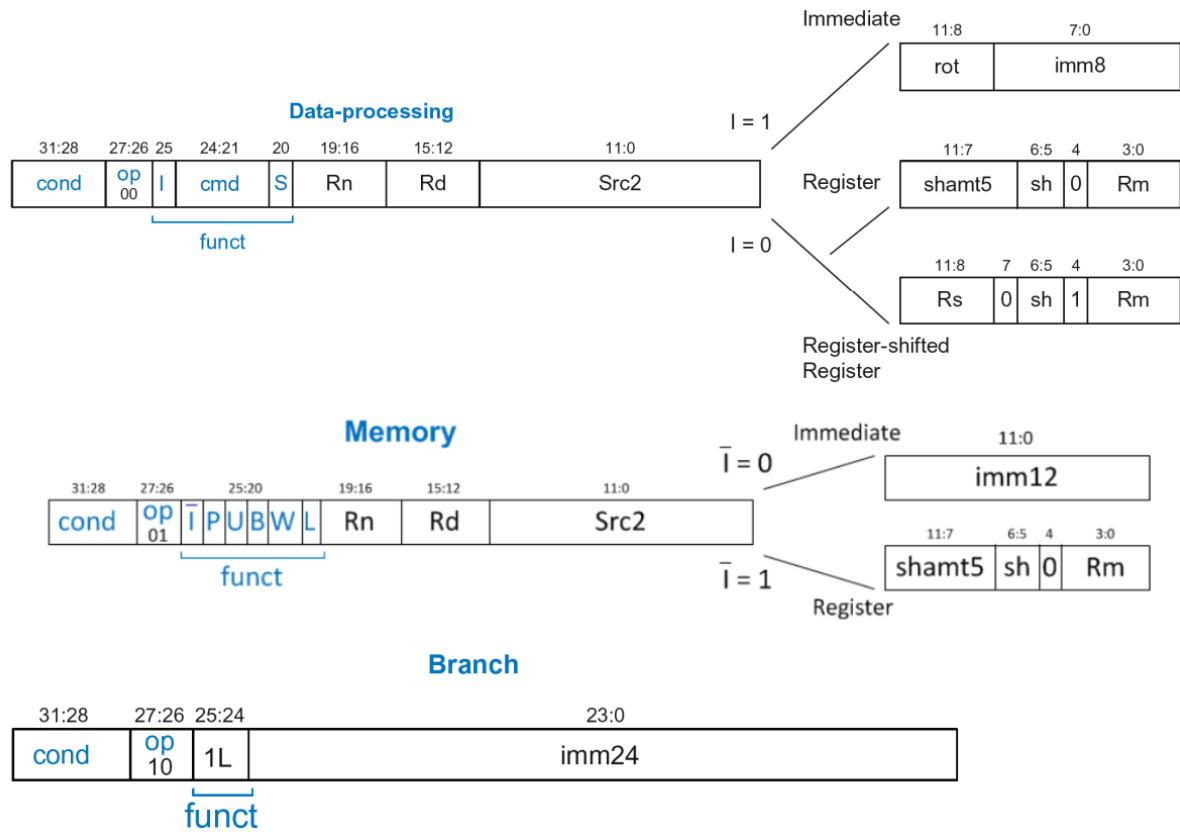


Figure 1: ARM ISA Format

1.2.1 Datapath Design (30% Credits)

In this part of the laboratory work, given your ISA, you are expected to design a full datapath to support all the instructions in the Table 1. The instructions will be stored in a unified instruction/data memory, IDM, read from and executed. Since instructions are read from the same memory that LDR/STR operations access, multi-cycle processor follows the Von Neumann architecture.

As stated in the previous subsection, the previous ALU can be used, without modification to operations, and control signal meanings can change (which would inherently affect the control signals required for the proper operation), although there should not be any need for it. As another design limitation, **you can use only a single arithmetic logic unit, and no wired connection between the ALU and the IDM is allowed**. Besides, you may as well use other functional components and registers for temporary data storage, provided that you support your reasoning. You are not allowed to design new modules like in the previous laboratory.

The design will extend the datapath we discussed in the lectures. A shifter needs to be added to support data processing instructions with shift. This shifter can also be used for branches, but we built in that functionality to the extender, as in lecture notes. Some modifications in the datapath connections are also needed for BL and BX instructions. ALU has a pass-through for the second operand that you can use for MOV.

Considering the instruction set provided in Table 1, perform the following design steps:

1. (20% Credits) Using Verilog HDL, implement the Datapath using only modules and wires; no additional logic is allowed. In your report, show the synthesized Datapath's RTL view. No I/O signal should be floating or have a constant value, indicating an error.
2. (10% Credits) In your report, explain how you added the functionalities not discussed in the lecture notes. The register shifted immediate operations, both MOV operations, BL and BX.

For the operation of the computer, a certain external signal, namely **RESET**, is also necessary. Reset resets the computer synchronously at the next positive clock edge. It should reset the architectural state including PC, register file and flags.

NOTE: To obtain a synthesized RTL schematic in Vivado, locate the Flow Navigator in the left of your screen. Then under RTL ANALYSIS, press Run Linter. Then expand Open Elaborated Design, and at the bottom, find Schematic and click on it. This will show the overall schematic, you need to find the module you want to show and expand it by clicking the plus on its top-left corner.

1.2.2 Controller Design (40% Credits)

The design of the control unit may be considered as designing the FSM (finite-state machine) that will generate the control sequence in the correct conditional and sequential order concerning the cycles described in the lecture notes.

- **C0: Fetch Cycle:** This is the first cycle corresponding to the operation of a single instruction. The instruction is read from the instruction/data memory to be loaded to an instruction register that holds the current one. Meanwhile, the program counter (PC) is increased to point to the next instruction.
- **C1: Decode Cycle:** Within the decode cycle, the current instruction in the instruction register is decoded to obtain the conditions and the operands.
- **C2: Execute and Branches Cycle:** In this cycle, the data is processed using the ALU or branch is taken.
- **C3: MemWrite/MemRead and ALU Writeback:** In this cycle, processed data is written back to the register file or to the memory.
- **C4: Memory Writeback:** In this cycle, data read from memory is written back to the register file.

For the supplied test bench to work, you must ensure your instruction types take the same number of cycles as in the lecture notes described in Figure 4. You are heavily encouraged to follow the lecture notes.

- Data Processing and Store instructions: 4 cycles
- Branch Instructions (BL and BX included): 3 cycles
- Load instructions: 5 cycles


Regarding the above-given descriptions, with support for new instructions and addressing modes, you must determine which control signal in your design is to be utilized in which cycle.

For the operation of the FSM, a certain external signal, namely **RESET** is also necessary.

- **RESET(active high)**: Terminates the operation and sets the FSM to the first state at the next positive clock edge.

Perform the following steps:

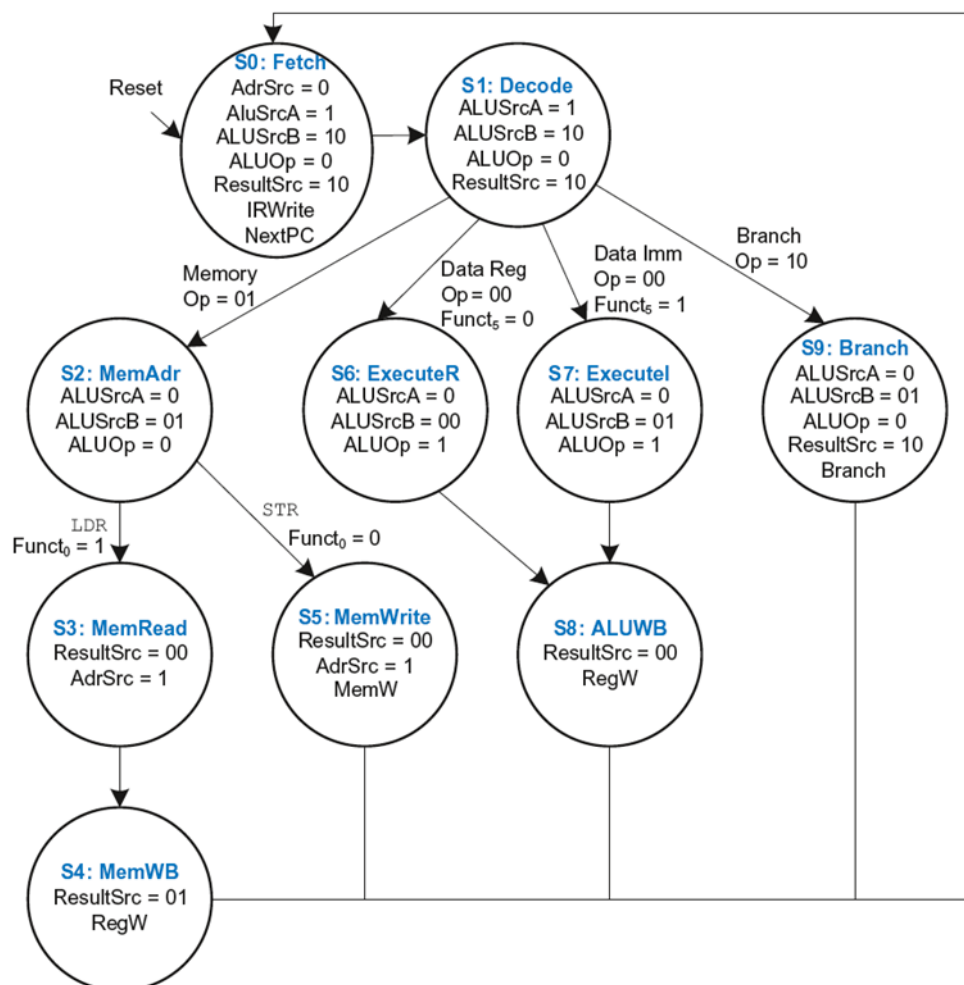1. (30% Credits) Using Verilog HDL, implement the Controller. There is no restriction, and you can write it however you like. In your report, show the synthesized Controller's RTL view. No I/O signal should be floating or have a constant value, as that indicates an error.
2. (10% Credits) In your report, explain how you added the functionalities not discussed in the lecture notes. The register shifted immediate operations, both MOV operations, BL and BX.



1.2.3 Top level for Tests (10% Credits)

Connect your Datapath and Controller in another module. This top module must have clock, reset and debug register select inputs. It must have outputs which are program counter, FSM State and the value of the register being debugged.

1.2.4 Testbench (20% Credits)

Now that you have completed the implementation of the multi-cycle CPU, it is required to verify its operation through some light programming. You will use the supplied testbench. **If the computer cannot execute at least the MOV immediate instruction in the testbench, you will not be admitted to the lab.**

Don't forget to give the proper signal handles to the initialization function of the testbench class. Also, you can fill in the log_controller and log_datapath functions inside the helper library for your debugging purposes. **Do not change anything inside the TB class**

Note that your design will fail the testbench if the number of clock cycles for each instruction does not match the specification given in subsection 1.2.2. Your report must include the test bench results as a screenshot!

2 Experimental Work

To upload your designs to the FPGA, you will use Vivado to create a project, with proper pin assignments using the master XDC file, and module initialization.

2.1 Multi Cycle Processor (100% Credits)

Load your processor designed in the Preliminary Work Part 1.2 to the Nexys A7 board. Load the instructions to your instruction memory using \$readmemh with the provided hex file.

Your proctoring assistant will check the design and grade you depending on how many instructions the computer can successfully execute. You can get help from the proctors, but any major help will decrease your performance grade.

You must use the supplied top-level file that will connect all the necessary signals to the board's buttons, switches, and seven-segment displays. Note that this file is different from the one used in Single Cycle Lab.

The supplied top-level file has the following connections:

1. Debug register select connects to the switches and debug register output connects to 5 seven-segments.
2. PC register connects to 2 seven-segments.
3. FSM's state connects to 1 seven-segment display for ease of debugging.

3 Parts List

Nexys A7 100T Board